
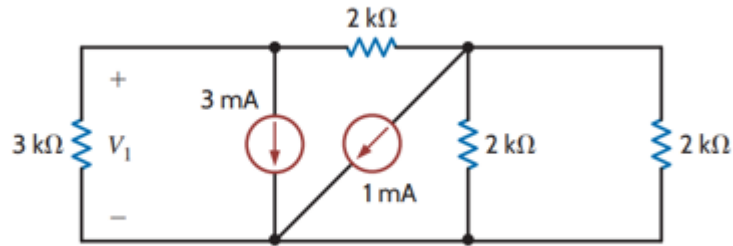


**3.1.19** Use nodal analysis to find  $V_1$  in the circuit in Fig. P3.1.19.

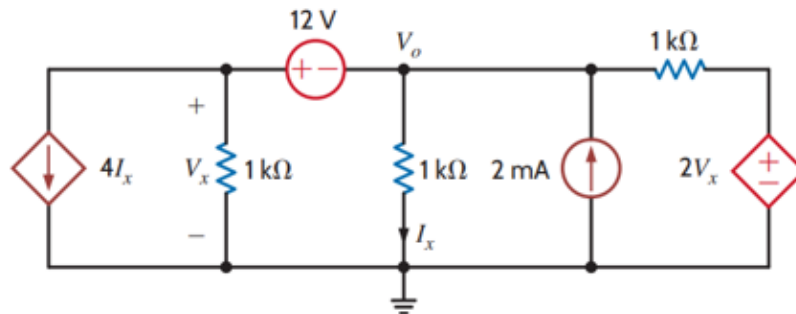


**FIGURE P3.1.19**

**3.1.40** Use nodal analysis to find  $V_o$  in the circuit in Fig. P3.1.40.




**FIGURE P3.1.40**

**3.1.45** Use nodal analysis to determine the node voltages defined in the circuit in Fig. P3.1.45.

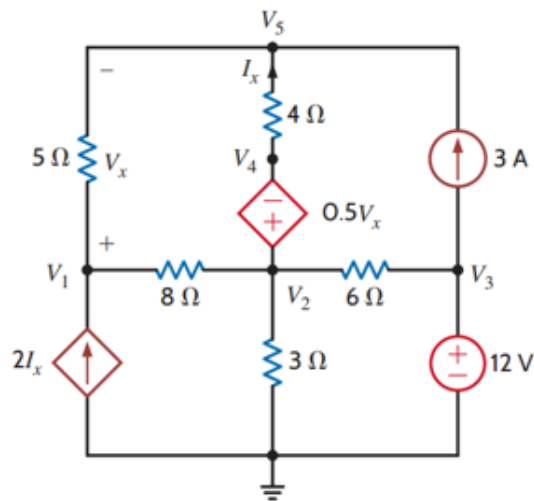


**FIGURE P3.1.45**

**3.2.15** Using loop analysis, find  $V_o$  in the circuit in Fig. P3.2.15.

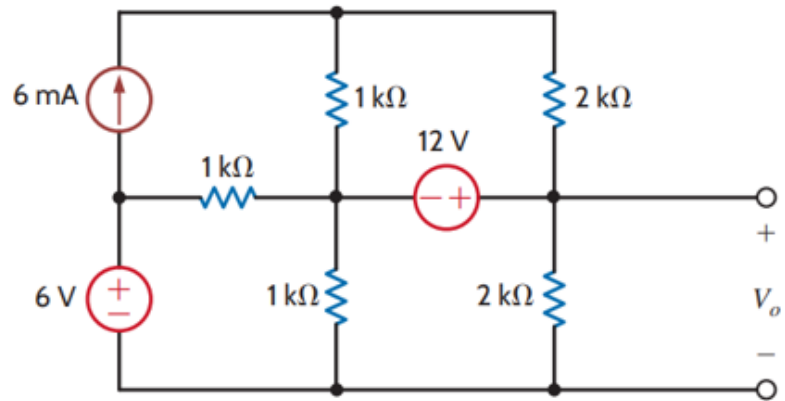


**FIGURE P3.2.15**

**3.2.16** Find  $I_o$  in the circuit in Fig. P3.2.16 using loop analysis.

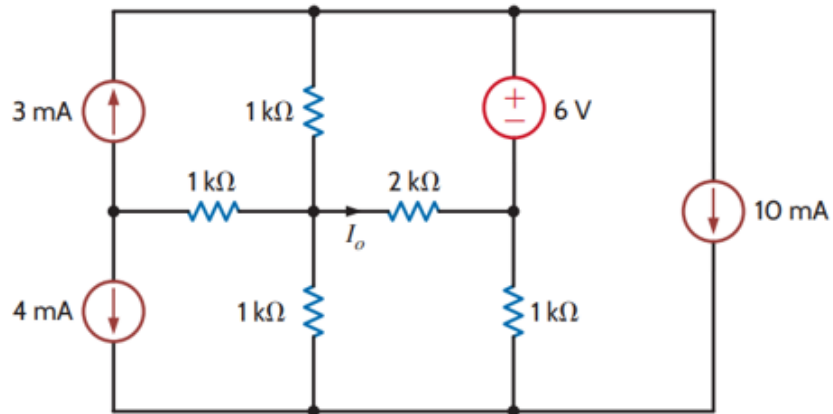


**FIGURE P3.2.16**

**3.2.22** Using loop analysis, find  $V_o$  in the network in Fig. P3.2.22.

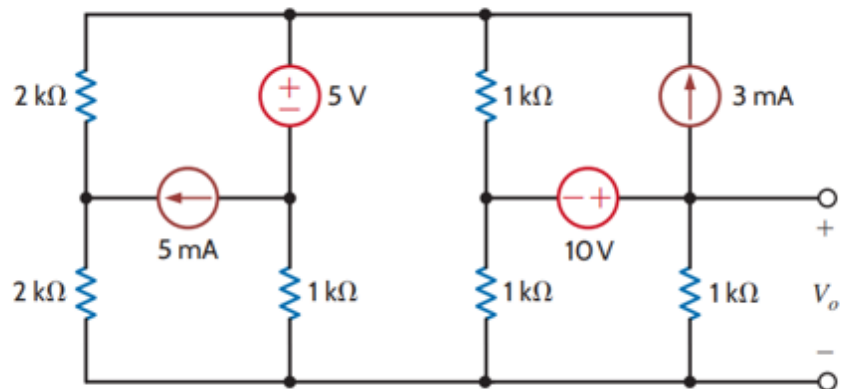


**FIGURE P3.2.22**

**3.2.26** Use both nodal analysis and mesh analysis to find  $V_o$  in the circuit in Fig. P3.2.26.

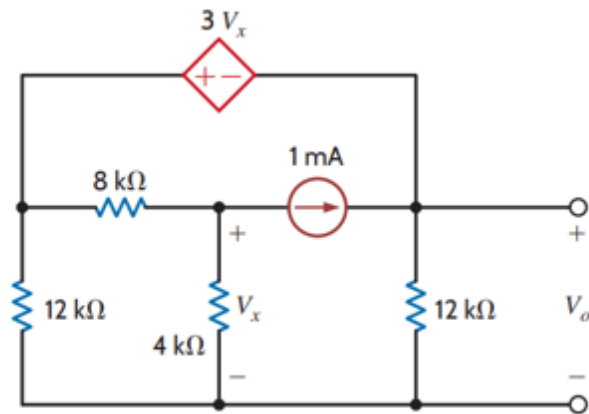

**FIGURE P3.2.26**

**3.2.34** Using loop analysis, find  $I_o$  in the network in Fig. P3.2.34.

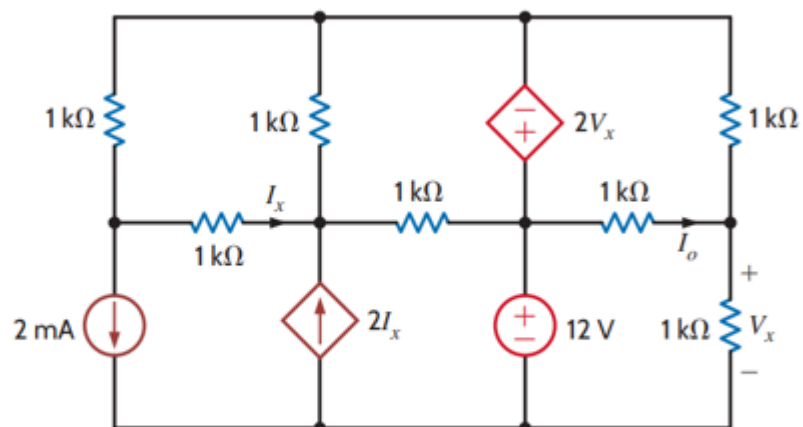

**FIGURE P3.2.34**